

Resonance in LCR circuit

Illustration of components:

Series circuit

Inductance Box

Capacitance Box

Resistance Box


Function Generator

Alternate Function Generator

Voltmeter

Parallel circuit

Series LCR circuit

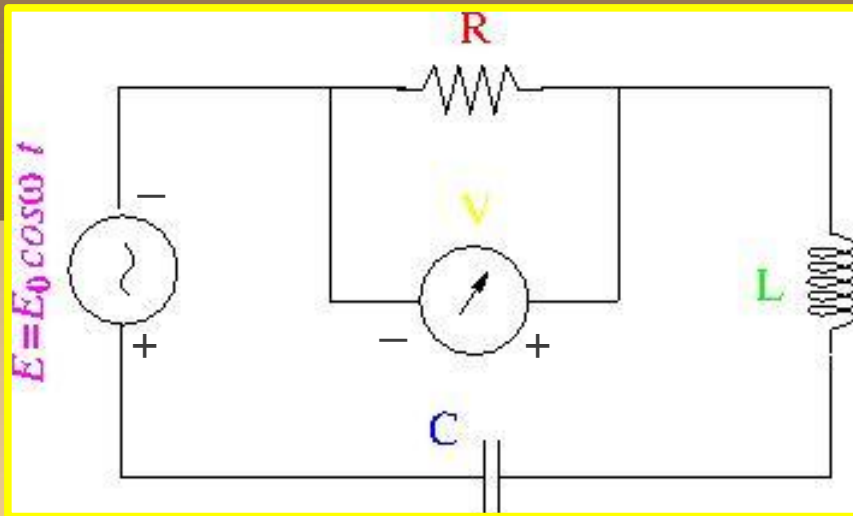


V: Voltmeter (reading AC voltage)

L: Inductor

C: Capacitor

E : Sinusoidal EMF through Function Generator

R: Resistance

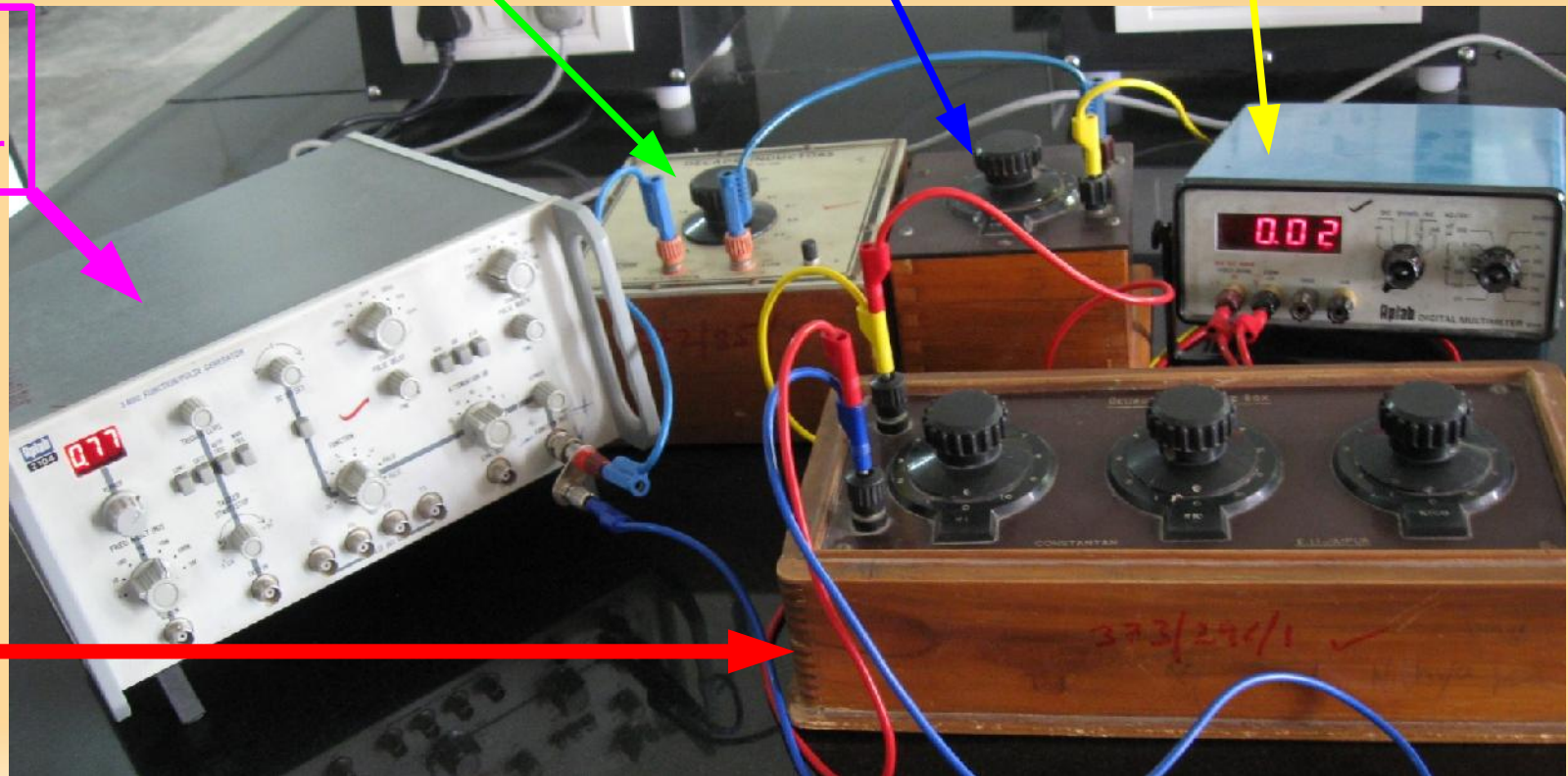

Inductor




Dial of Inductance Box
adjusted to 10:

$$L = 10 \times 0.001 \text{ H}$$


Capacitor

Dial of Capacitance Box
adjusted to 1:

$$C = 1 \times 0.1 \text{ micro-Farad}$$

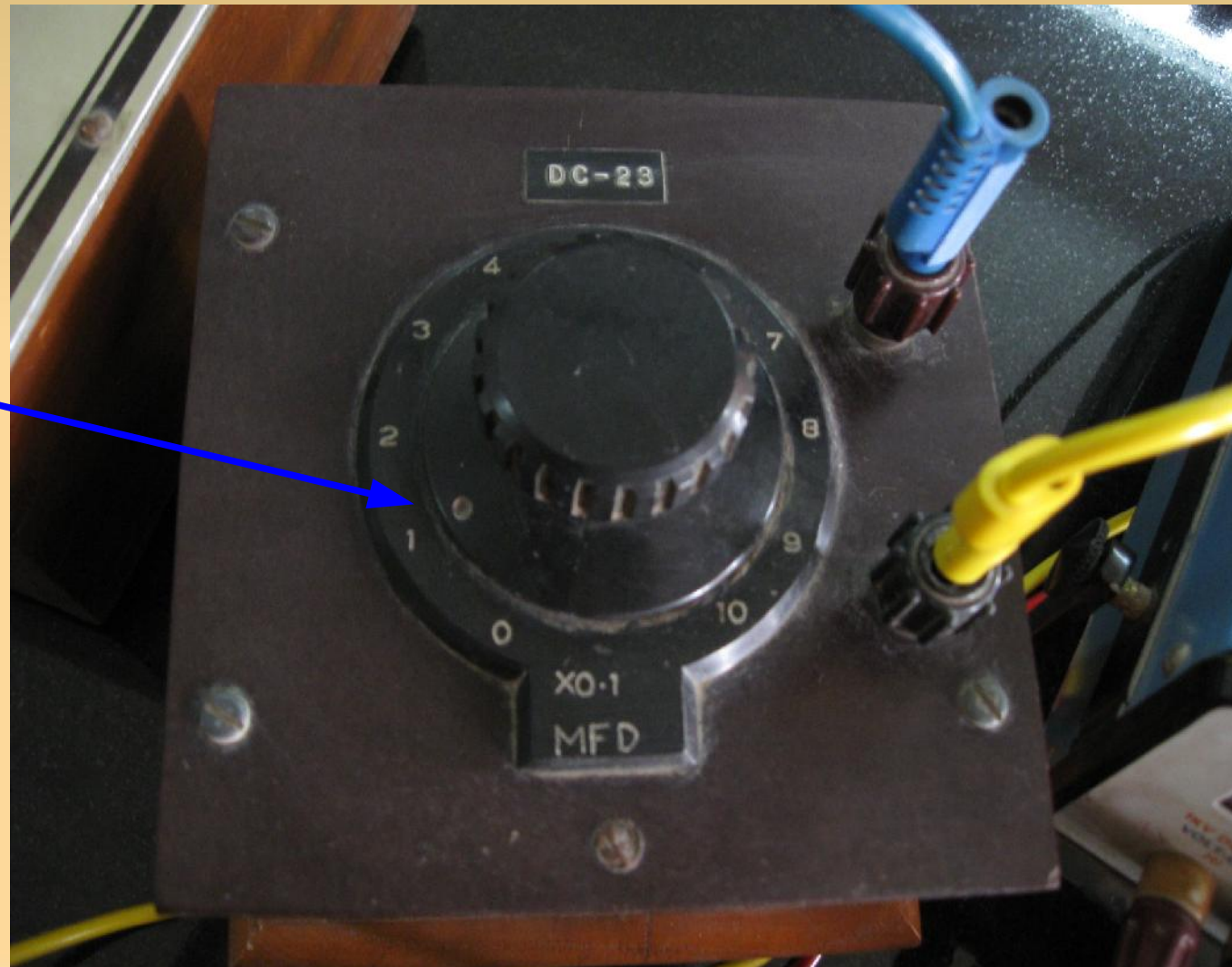


Resistance

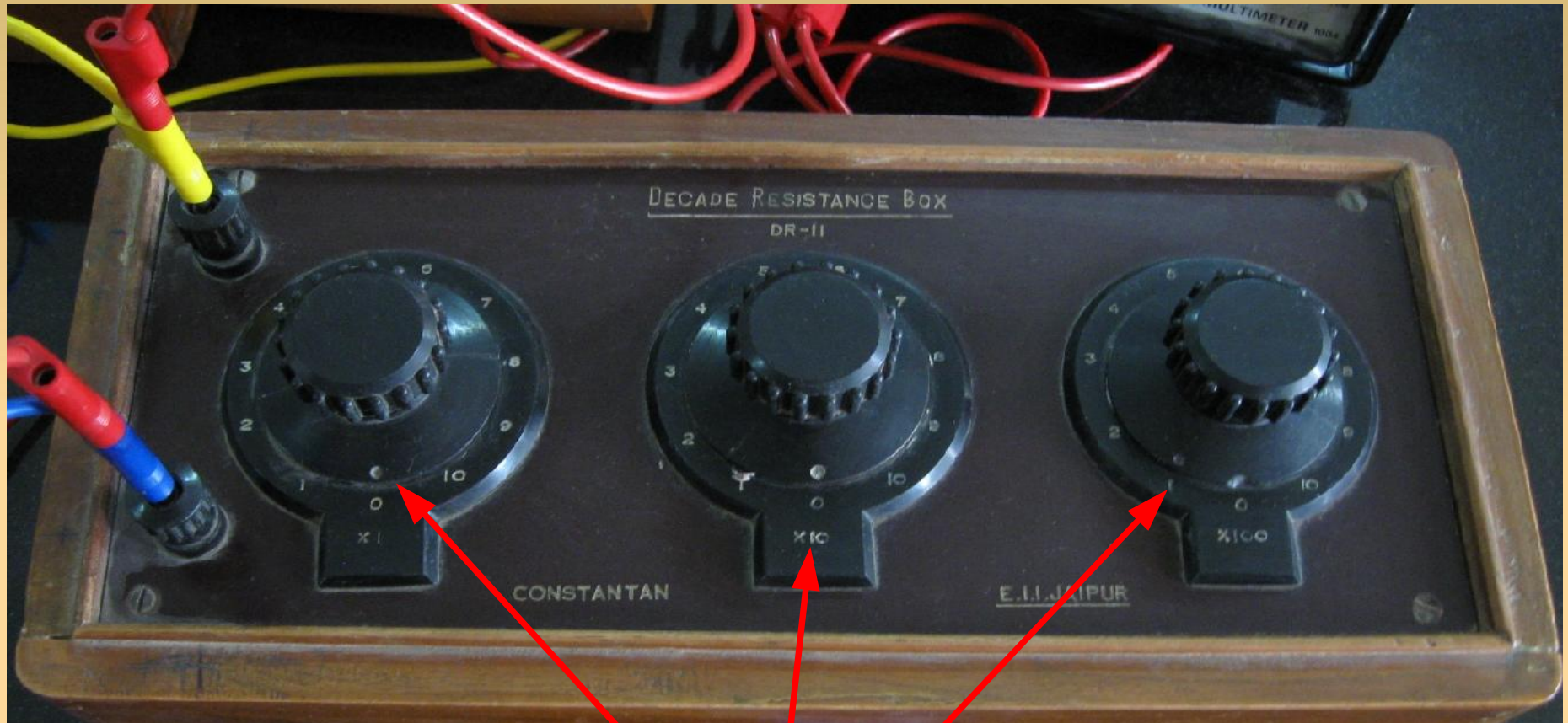

Dials of Resistance Box adjusted to 0, 0, 1: $R = 0 \times 1 + 0 \times 10 + 1 \times 100 = 100 \text{ ohm}$

Function Generator

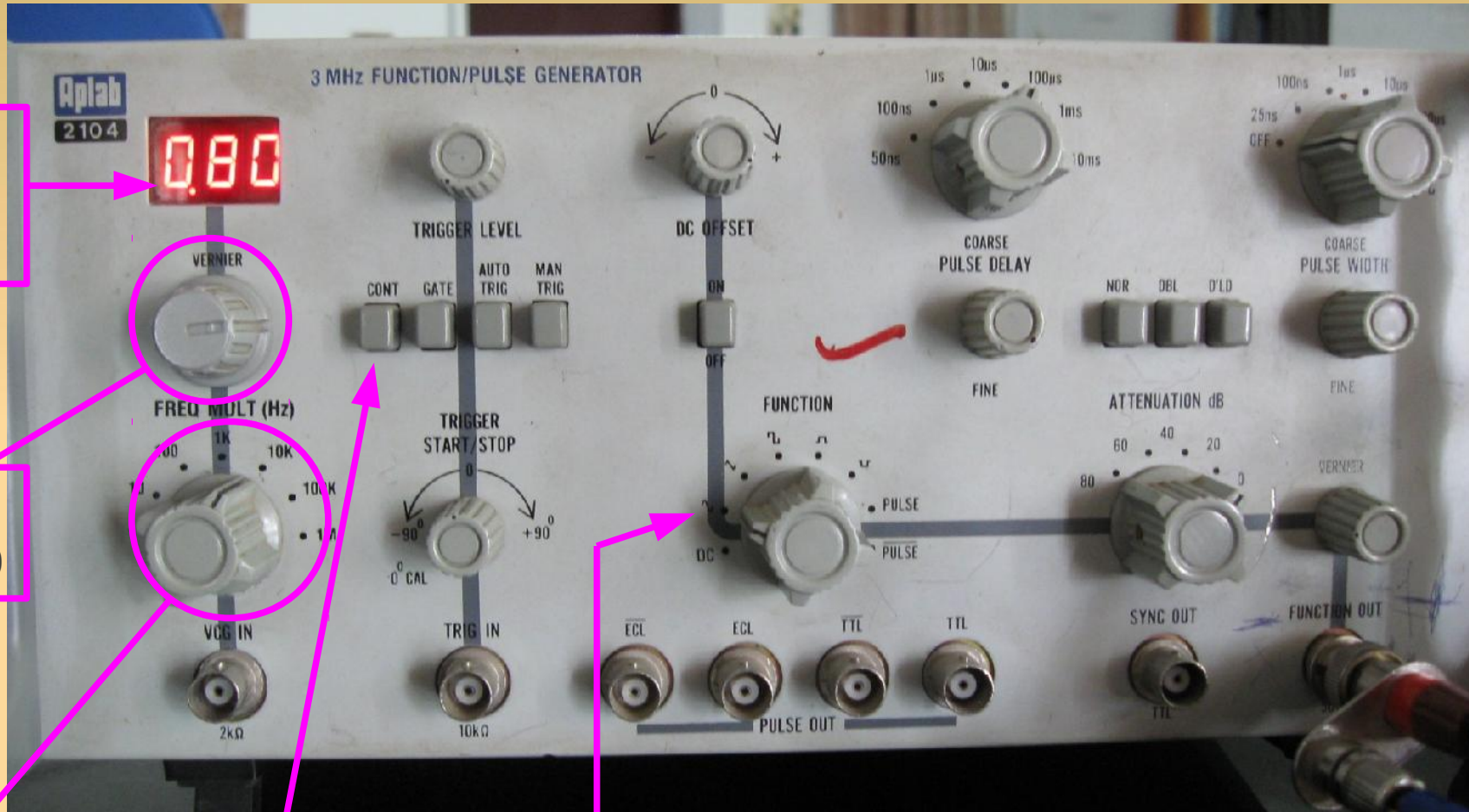

Frequency:
 $f = 0.8 \times 10 \text{ kHz}$
 $= 8 \text{ kHz}$

Vernier dial
rotated to 0.80

Frequency Range
set to 10 kHz

Function type adjusted to sinusoid

Continuous mode requires to be used

Alternate Function Generator

Frequency range to be selected

Sinusoid to be selected



Vernier dial

Frequency $f =$ Value on vernier dial
 \times Value of frequency multiplier

Voltmeter

(multimeter used as voltmeter)

Voltage across the resistance $V = 1.23$ volt

Precision Adjustmet

1.23

DC OHMS AC AC/DC
mA V V mA mV 200
 μ A 2 20 20K
V 200 2M
1000 20M
OFF

1KV DC MAX
VOLT-OHM
HI

COM
LO

GND

mA

Rplab DIGITAL MULTIMETER 1004

To be connected to the two ends of the Resistance box

Dial indicates measurement of AC voltage

Numbers indicate maximum voltage that can be read: set to 20 volt

Parallel LCR circuit

Using the same components the **SERIES** circuit can be changed into **PARALLEL** by rearranging the connecting wires.

